

DIGITAL DESIGN (CSET-105)

Assignment – Mux-Demux

NAME:- Aryan Gahlot

Enrolment no. :- S24CSEU0701

BATCH NO. :- 43

Q1) What is multiplexer? Discuss in brief with appropriate block diagram and examples.

Answer:


A **Multiplexer (MUX)** is a combinational circuit that selects one of the multiple input signals and forwards the selected input to a single output line. It acts as a data selector, allowing multiple signals to share a single transmission line.

Block Diagram of a Multiplexer

A general **n-to-1** multiplexer has:

A general **n-to-1** multiplexer has:

 - **n input lines** ($I_0, I_1, I_2, \dots, I_{n-1}$)
- **m selection lines** (S_0, S_1, \dots, S_{m-1}) where $m = \log_2 n$
- **1 output line** (Y)



S1	S0	Y(Output)
0	0	I0
0	1	I1
1	0	I2
1	1	I3

Examples of Multiplexers


1. **Communication Systems:** Used to transmit multiple signals over a single communication channel.
2. **Data Routing:** Used in computer networks to switch between different data sources.
3. **Arithmetic and Logic Units (ALU):** Used in processors to select operations.
4. **Memory Access:** Helps in selecting data from different memory locations.

Q2) What is Demultiplexer? Discuss in brief with appropriate block diagram and examples.

Answer:

A **Demultiplexer (DEMUX)** is a combinational circuit that takes a single input and directs it to one of the multiple output lines based on the selection inputs. It performs the reverse operation of a **Multiplexer (MUX)** and is often called a **data distributor**.

 - 1 input line (D)
- m selection lines (S_0, S_1, \dots, S_{m-1}) where $m = \log_2 n$
- n output lines ($Y_0, Y_1, Y_2, \dots, Y_{n-1}$)



S1	S0	Output
0	0	Y0
0	1	Y1
1	0	Y2
1	1	Y3

Examples of Demultiplexers

1. **Communication Systems:** Used to route a single incoming signal to multiple destinations.
2. **Memory Selection:** Used in RAM for selecting specific memory locations.
3. **Arithmetic Circuits:** Used in ALUs to distribute results to different registers.
4. **Serial to Parallel Data Conversion:** Used to convert serial data (one input) into parallel outputs.

Q3)Write truth table and Verilog code to implement 2:1 Multiplexer.

Answer:

```
[2025-02-24 11:28:56 UTC] iverilog '-wall' '-g2012' design.sv testbench.sv && unbuffer vvp a.out
VCD info: dumpfile multiplexer_2to1.vcd opened for output.
Io I1 S | Y
-----
0 0 0 | 0
1 0 0 | 1
0 1 0 | 0
1 1 0 | 1
0 0 1 | 0
1 0 1 | 0
0 1 1 | 1
1 1 1 | 1
testbench.sv:29: $finish called at 80 (1s)
Finding VCD file...
./multiplexer_2to1.vcd
[2025-02-24 11:28:57 UTC] Opening EPWave...
Done
```

Design:

```
module multiplexer_2to1 (input wire Io, input wire I1, input wire S,output wire Y);
```

```
assign Y = (~S&Io)|(S&I1);
```

```
endmodule
```

Testbench:

```
module tb_multiplexer_2to1;
```

```
    reg Io;
```

```
    reg I1;
```

```
    reg S;
```

```
    wire Y;
```

```
    multiplexer_2to1 uut (.Io(Io), .I1(I1), .S(S), .Y(Y));
```

initial begin

```
$dumpfile("multiplexer_2to1.vcd");
```

```
$dumpvars(0, tb_multiplexer_2to1);
```

```
$display("lo l1 S | Y");
```

```
$display("-----");
```

```
$monitor("%b %b %b | %b", lo, l1, S, Y);
```

```
S = 0; lo = 0; l1 = 0; #10;
```

```
S = 0; lo = 1; l1 = 0; #10;
```

```
S = 0; lo = 0; l1 = 1; #10;
```

```
S = 0; lo = 1; l1 = 1; #10;
```

```
S = 1; lo = 0; l1 = 0; #10;
```

```
S = 1; lo = 1; l1 = 0; #10;
```

```
S = 1; lo = 0; l1 = 1; #10;
```


```
S = 1; lo = 1; l1 = 1; #10;
```

```
$finish;
```

end

endmodule

Waveform:

 

Q4) Write truth table and Verilog code to implement 1:4 Demultiplexer.

Answer:

```
[2025-02-24 11:36:08 UTC] iverilog '-wall' '-g2012' design.sv testbench.sv && unbuffer vvp a.out
```

VCD info: dumpfile demultiplexer_4to1.vcd opened for output.

```
I  S1 S0 | Y0 Y1 Y2 Y3
```

```
-----
```

```
1 0 0 | 1 0 0 0
```

```
1 0 1 | 0 1 0 0
```

```
1 1 0 | 0 0 1 0
```

```
1 1 1 | 0 0 0 1
```

```
0 0 0 | 0 0 0 0
```

```
0 0 1 | 0 0 0 0
```

```
0 1 0 | 0 0 0 0
```

```
0 1 1 | 0 0 0 0
```

```
testbench.sv:37: $finish called at 80 (1s)
```

```
Finding VCD file...
```

```
./demultiplexer_4to1.vcd
```

```
[2025-02-24 11:36:09 UTC] Opening EPWave...
```

```
Done
```

Design:

```
module demultiplexer_4to1 (input wire I,input wire S0,input wire S1,output wire Y0,  
    output wire Y1,output wire Y2,output wire Y3);
```

```
    assign Y0 = (~S1 & ~S0 & I);
```

```
    assign Y1 = (~S1 & S0 & I);
```

```
    assign Y2 = ( S1 & ~S0 & I);
```

```
    assign Y3 = ( S1 & S0 & I);
```

```
endmodule
```

Testbench:

```
module tb_demultiplexer_4to1;
```

```
reg I;
```

```
reg S0;
```

```
reg S1;
```

```
wire Y0, Y1, Y2, Y3;
```

```
demultiplexer_4to1 uut (
```

```
    .I(I),
```

```
    .S0(S0),
```

```
    .S1(S1),
```

```
    .Y0(Y0),
```

```
    .Y1(Y1),
```

```
    .Y2(Y2),
```

```
    .Y3(Y3)
```

```
);
```

```
initial begin
```

```
    $dumpfile("demultiplexer_4to1.vcd");
```

```
    $dumpvars(0, tb_demultiplexer_4to1);
```

```
    $display(" I  S1 S0 | Y0 Y1 Y2 Y3");
```

```
    $display("-----");
```

```
    $monitor("%b %b %b | %b %b %b %b", I, S1, S0, Y0, Y1, Y2, Y3);
```

I = 1; S1 = 0; S0 = 0; #10;

I = 1; S1 = 0; S0 = 1; #10;

I = 1; S1 = 1; S0 = 0; #10;

I = 1; S1 = 1; S0 = 1; #10;

I = 0; S1 = 0; S0 = 0; #10;

I = 0; S1 = 0; S0 = 1; #10;

I = 0; S1 = 1; S0 = 0; #10;


I = 0; S1 = 1; S0 = 1; #10;

\$finish;

end

endmodule

Waveform:

 

Q 5) Implement the Boolean function $F(A, B, C) = \sum m(3, 5, 6, 7)$ with a 4:1 multiplexer. Write a Verilog code for the above design

Answer:

A	B	C	F(A,B,C)
0	0	0	0

0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Design:

```
module mux4to1 (
```

```
    input wire A, B, C,
```

```
    output wire F
```

```
);
```

```
    wire S1, S0;
```

```
    assign S1 = A;
```

```
    assign S0 = B;
```

```
    wire I0, I1, I2, I3;
```

```
    assign I0 = 0;
```

```
    assign I1 = C;
```

```
    assign I2 = C;
```

```
    assign I3 = 1;
```

```
    assign F = (~S1 & ~S0 & I0) |
```

```
        (~S1 & S0 & I1) |
```

```
        (S1 & ~S0 & I2) |
```

```
        (S1 & S0 & I3);
```

```
endmodule
```


Testbench:

```
module tb_mux4to1;

    reg A, B, C;

    wire F;

    mux4to1 uut (.A(A), .B(B), .C(C), .F(F));

    initial begin

        $monitor("A=%b, B=%b, C=%b -> F=%b", A, B, C, F);

        A = 0; B = 0; C = 0; #10;
        A = 0; B = 0; C = 1; #10;
        A = 0; B = 1; C = 0; #10;
        A = 0; B = 1; C = 1; #10;
        A = 1; B = 0; C = 0; #10;
        A = 1; B = 0; C = 1; #10;
        A = 1; B = 1; C = 0; #10;
        A = 1; B = 1; C = 1; #10;

        $finish;

    end

endmodule
```